

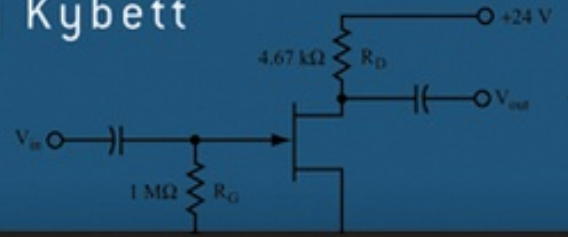


Earl Boysen + Harry Kybett

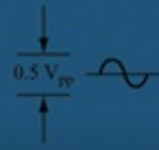

# COMPLETE ELECTRONICS SELF-TEACHING GUIDE

with Projects

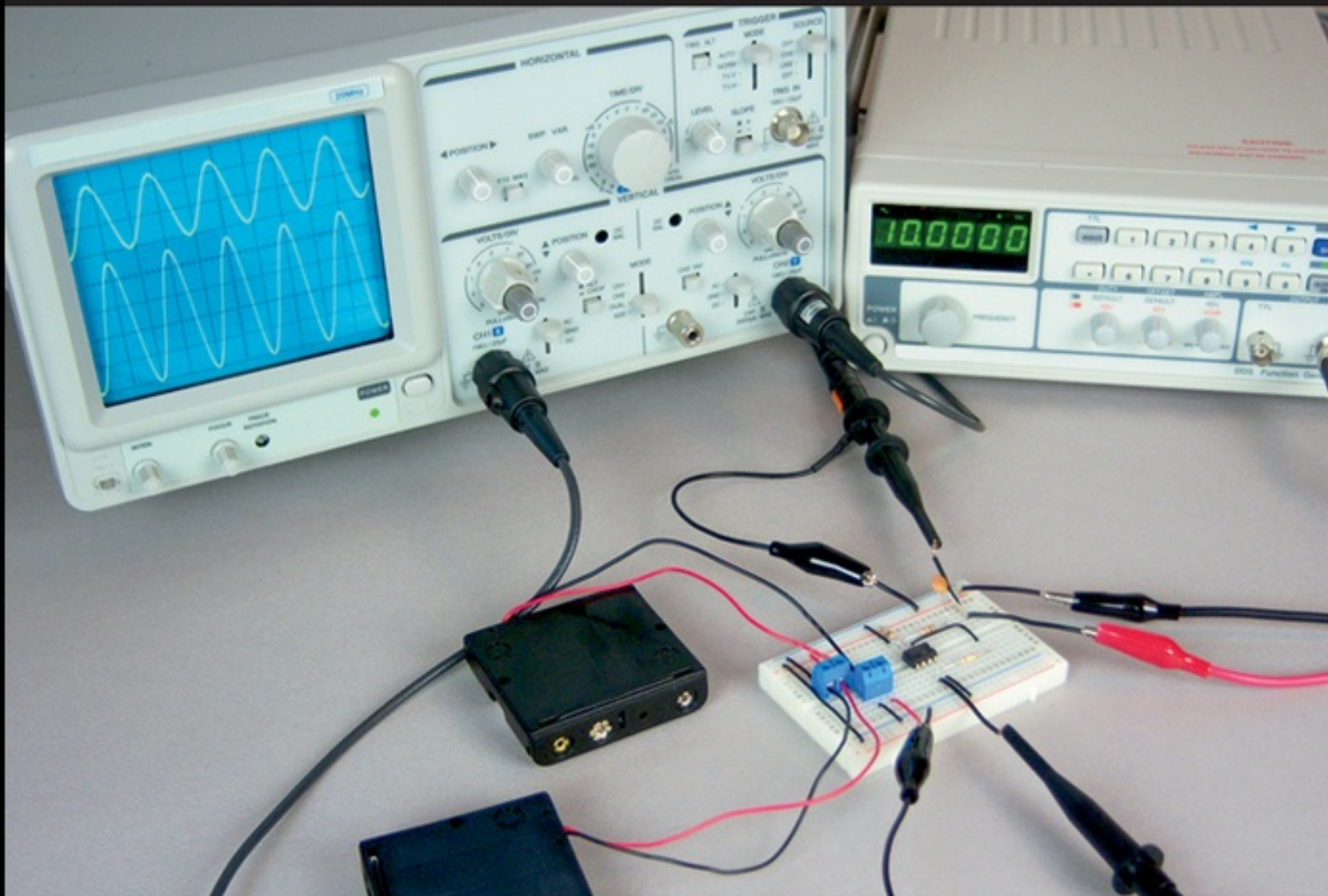

# Table of Contents

---

## Chapter 1: DC Review and Pre-Test

Current Flow

Ohm's Law

Resistors in Series

Resistors in Parallel

Power

Small Currents

The Graph of Resistance

The Voltage Divider

The Current Divider

Switches

Capacitors in a DC Circuit

Summary

DC Pre-Test

## Chapter 2: The Diode

Understanding Diodes

Diode Breakdown

The Zener Diode

Summary

Self-Test

## Chapter 3: Introduction to the Transistor

Understanding Transistors

The Junction Field Effect Transistor (JFET)

Summary

Self-Test

## Chapter 4: The Transistor Switch

[Turning the Transistor On](#)

---

[Turning Off the Transistor](#)

[Why Transistors Are Used as Switches](#)

[The Three-Transistor Switch](#)

[Alternative Base Switching](#)

[Switching the JFET](#)

[Summary](#)

[Self-Test](#)

## [Chapter 5: AC Pre-Test and Review](#)

[The Generator](#)

[Resistors in AC Circuits](#)

[Capacitors in AC Circuits](#)

[The Inductor in an AC Circuit](#)

[Resonance](#)

[Summary](#)

[Self-Test](#)

## [Chapter 6: Filters](#)

[Capacitors in AC Circuits](#)

[Capacitors and Resistors in Series](#)

[Phase Shift of an RC Circuit](#)

[Resistor and Capacitor in Parallel](#)

[Inductors in AC Circuits](#)

[Phase Shift for an RL Circuit](#)

[Summary](#)

[Self-Test](#)

## [Chapter 7: Resonant Circuits](#)

[The Capacitor and Inductor in Series](#)

[The Output Curve](#)

## [Introduction to Oscillators](#)

---

[Summary](#)

[Self-Test](#)

## [Chapter 8: Transistor Amplifiers](#)

[Working with Transistor Amplifiers](#)

[A Stable Amplifier](#)

[Biasing](#)

[The Emitter Follower](#)

[Analyzing an Amplifier](#)

[The JFET as an Amplifier](#)

[The Operational Amplifier](#)

[Summary](#)

[Self-Test](#)

## [Chapter 9: Oscillators](#)

[Understanding Oscillators](#)

[Feedback](#)

[The Colpitts Oscillator](#)

[The Hartley Oscillator](#)

[The Armstrong Oscillator](#)

[Practical Oscillator Design](#)

[Simple Oscillator Design Procedure](#)

[Oscillator Troubleshooting Checklist](#)

[Summary and Applications](#)

[Self-Test](#)

## [Chapter 10: The Transformer](#)

[Transformer Basics](#)

[Transformers in Communications Circuits](#)

[Summary and Applications](#)

[Self-Test](#)

---

[Answers to Self-Test](#)

[Chapter 11: Power Supply Circuits](#)

[Diodes in AC Circuits Produce Pulsating DC](#)

[Level DC \(Smoothing Pulsating DC\)](#)

[Summary](#)

[Self-Test](#)

[Chapter 12: Conclusion and Final Self-Test](#)

[Conclusion](#)

[Final Self-Test](#)

[Appendix A: Glossary](#)

[Appendix B: List of Symbols and Abbreviations](#)

[Appendix C: Powers of Ten and Engineering Prefixes](#)

[Appendix D: Standard Composition Resistor Values](#)

[Appendix E: Supplemental Resources](#)

[Web Sites](#)

[Books](#)

[Magazines](#)

[Suppliers](#)

[Appendix F: Equation Reference](#)

[Appendix G: Schematic Symbols Used in This Book](#)

[Introduction](#)

[What This Book Teaches](#)

[How This Book Is Organized](#)

## Conventions Used in This Book

---

### How to Use This Book

## DC Review and Pre-Test

Electronics cannot be studied without first understanding the basics of electricity. This chapter is a review and pre-test on those aspects of direct current (DC) that apply to electronics. By no means does it cover the whole DC theory, but merely those topics that are essential to simple electronics.

This chapter reviews the following:

- Current flow
- Potential or voltage difference
- Ohm's law
- Resistors in series and parallel
- Power
- Small currents
- Resistance graphs
- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- Voltage and current dividers
- Switches
- Capacitor charging and discharging
- Capacitors in series and parallel

## Current Flow

**1** Electrical and electronic devices work because of an electric current.

### Question

What is an electric current?

### Answer

An *electric current* is a flow of electric charge. The electric charge usually consists of negatively charged electrons. However, in semiconductors, there are also positive charge carriers called *holes*.

**2** There are several methods that can be used to generate an electric current.

### Question

Write at least three ways an electron flow (or current) can be generated.

## Answer

The following is a list of the most common ways to generate current:

- *Magnetically*—This includes the induction of electrons in a wire rotating within a magnetic field. An example of this would be generators turned by water, wind, or steam, or the fan belt in a car.
- *Chemically*—This involves the electrochemical generation of electrons by reactions between chemicals and electrodes (as in batteries).
- *Photovoltaic generation of electrons*—This occurs when light strikes semiconductor crystals (as in solar cells).

Less common methods to generate an electric current include the following:

- *Thermal generation*—This uses temperature differences between thermocouple junctions. Thermal generation is used in generators on spacecrafts that are fueled by radioactive material.
- *Electrochemical reaction*—This occurs between hydrogen, oxygen, and electrodes (fuel cells).
- *Piezoelectrical*—This involves mechanical deformation of piezoelectric substances. For example, piezoelectric material in the heels of shoes power LEDs that light up when you walk.

**3** Most of the simple examples in this book contain a battery as the voltage source. As such, the source provides a potential difference to a circuit that enables a current to flow. An *electric current* is a flow of electric charge. In the case of a battery, electrons are the electric charge, and they flow from the terminal that has an excess number of electrons to the terminal that has a deficiency of electrons. This flow takes place in any complete circuit that is connected to battery terminals. It is the difference in the charge that creates the potential difference in the battery. The electrons try to balance the difference.

Because electrons have a negative charge, they actually flow from the negative terminal and return to the positive terminal. This direction of flow is called *electron flow*. Most books, however, use *current flow*, which is in the opposite direction. It is referred to as *conventional current flow*, or simply current flow. In this book, the term conventional current flow is used in all circuits.


Later in this book, you see that many semiconductor devices have a symbol that contains an arrowhead pointing in the direction of conventional current flow.



## Questions

A. Draw arrows to show the current flow in [Figure 1.1](#). The symbol for the battery shows its polarity.

[Figure 1.1](#)

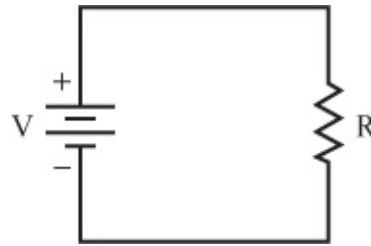

B. What indicates that a potential difference is present? \_\_\_\_\_


C. What does the potential difference cause? \_\_\_\_\_

D. What will happen if the battery is reversed? \_\_\_\_\_

## Answers

A. See [Figure 1.2](#).

[Figure 1.2](#)

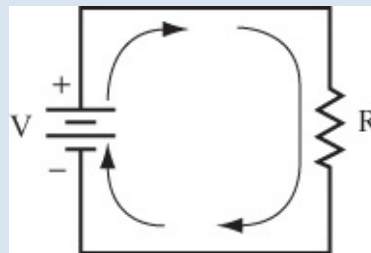

B. The battery symbol indicates that a difference of potential (also called *voltage*) is being supplied to the circuit.

C. Voltage causes current to flow if there is a complete circuit present, as shown in [Figure 1.1](#).

D. The current flows in the opposite direction.

## Ohm's Law

4 Ohm's law states the fundamental relationship between voltage, current, and resistance.

### Question

What is the algebraic formula for Ohm's law? \_\_\_\_\_

## Answer

$$V = I \times R$$

This is the most basic equation in electricity, and you should know it well. Some electronics books state Ohm's law as  $E = IR$ .  $E$  and  $V$  are both symbols for voltage. This book uses  $V$  to indicate voltage. When  $V$  is used after a number in equations and circuit diagrams, it represents volts, the unit of measurement of voltage. Also, in this formula, resistance is the opposition to current flow. Large resistance results in smaller current for any given voltage.

**5** Use Ohm's law to find the answers in this problem.

## Questions

What is the voltage for each combination of resistance and current values?

**A.**  $R = 20$  ohms,  $I = 0.5$  amperes

$$V = \underline{\hspace{2cm}}$$

**B.**  $R = 560$  ohms,  $I = 0.02$  amperes

$$V = \underline{\hspace{2cm}}$$

**C.**  $R = 1,000$  ohms,  $I = 0.01$  amperes

$$V = \underline{\hspace{2cm}}$$

**D.**  $R = 20$  ohms  $I = 1.5$  amperes

$$V = \underline{\hspace{2cm}}$$

## Answers

**A.** 10 volts

**B.** 11.2 volts

**C.** 10 volts

**D.** 30 volts

**6** You can rearrange Ohm's law to calculate current values.

## Questions

What is the current for each combination of voltage and resistance values?

**A.**  $V = 1$  volt,  $R = 2$  ohms

$I =$  \_\_\_\_\_

**B.**  $V = 2$  volts,  $R = 10$  ohms

$I =$  \_\_\_\_\_

**C.**  $V = 10$  volts,  $R = 3$  ohms

$I =$  \_\_\_\_\_

**D.**  $V = 120$  volts,  $R = 100$  ohms

$I =$  \_\_\_\_\_

## Answers

**A.** 0.5 amperes

**B.** 0.2 amperes

**C.** 3.3 amperes

**D.** 1.2 amperes

**7** You can rearrange Ohm's law to calculate resistance values.

## Questions

What is the resistance for each combination of voltage and current values?

**A.**  $V = 1$  volt,  $I = 1$  ampere

$R =$  \_\_\_\_\_

**B.**  $V = 2$  volts,  $I = 0.5$  ampere

$R =$  \_\_\_\_\_

**C.**  $V = 10$  volts,  $I = 3$  amperes

$R =$  \_\_\_\_\_

**D.**  $V = 50$  volts,  $I = 20$  amperes

$R =$  \_\_\_\_\_

## Answers

**A.** 1 ohm

**B.** 4 ohms

**C.** 3.3 ohms

**D.** 2.5 ohms

**8** Work through these examples. In each case, two factors are given and you must find the third.

## Questions

What are the missing values?

- A. 12 volts and 10 ohms. Find the current. \_\_\_\_\_
- B. 24 volts and 8 amperes. Find the resistance. \_\_\_\_\_
- C. 5 amperes and 75 ohms. Find the voltage. \_\_\_\_\_

## Answers

- A. 1.2 amperes
- B. 3 ohms
- C. 375 volts

### Inside the Resistor

*Resistors* are used to control the current that flows through a portion of a circuit. You can use Ohm's law to select the value of a resistor that gives you the correct current in a circuit. For a given voltage, the current flowing through a circuit increases when using smaller resistor values and decreases when using larger resistor values.


This resistor value works something like pipes that run water through a plumbing system. For example, to deliver the large water flow required by your water heater, you might use a 1-inch diameter pipe. To connect a bathroom sink to the water supply requires much smaller water flow and therefore, works with a 1/2-inch pipe. In the same way, smaller resistor values (meaning less resistance) increase current flow, whereas larger resistor values (meaning more resistance) decrease the flow.

*Tolerance* refers to how precise a stated resistor value is. When you buy *fixed resistors* (in contrast to *variable resistors* that are used in some of the projects in this book), they have a particular resistance value. Their tolerance tells you how close to that value their resistance will be. For example, a 1,000-ohm resistor with  $\pm 5$  percent tolerance could have a value of anywhere from 950 ohms to 1,050 ohms. A 1,000-ohm resistor with  $\pm 1$  percent tolerance (referred to as a *precision resistor*) could have a value ranging anywhere from 990 ohms to 1,010 ohms. Although you are assured that the resistance of a precision resistor will be close to its stated value, the resistor with  $\pm 1$  percent tolerance costs more to manufacture and, therefore, costs you more than twice as much as a resistor with  $\pm 5$  percent tolerance. Most electronic circuits are designed to work with resistors with  $\pm 5$  percent tolerance. The most commonly used type of resistor with  $\pm 5$  percent tolerance is called a *carbon film resistor*. This term refers to the manufacturing process in which a carbon film is deposited on an insulator. The thickness and width of the carbon film determines the resistance (the thicker the carbon film, the lower the resistance). Carbon film resistors work well in all the projects in this book.

On the other hand, precision resistors contain a metal film deposited on an insulator. The thickness and width of the metal film determines the resistance. These resistors are called *metal film resistors* and are used in circuits for precision devices such as test instruments.

Resistors are marked with four or five color bands to show the value and tolerance of the resistor, as illustrated in the following figure. The four-band color code is used for most resistors. As shown in the figure, by adding a fifth band, you get a five-band color code. Five-band color codes are used

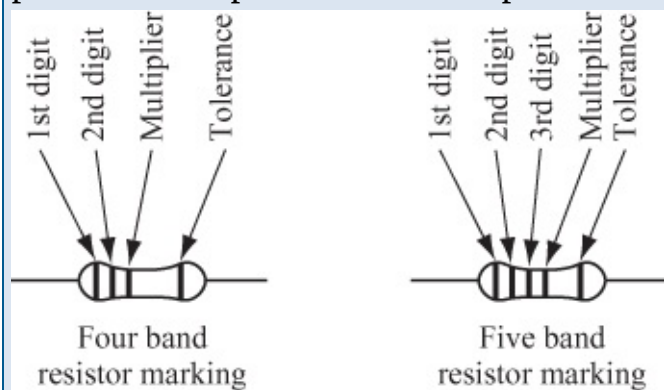provide more precise values in precision resistors.



The following table shows the value of each color used in the bands:


Color	Significant Digits	Multiplier	Tolerance
Black	0	1	
Brown	1	10	± 1 percent
Red	2	100	± 2 percent
Orange	3	1,000	
Yellow	4	10,000	
Green	5	100,000	
Blue	6	1,000,000	
Violet	7		
Gray	8		
White	9		
Gold		0.1	± 5 percent
Silver		0.01	± 10 percent

By studying this table, you can see how this code works. For example, if a resistor is marked with orange, blue, brown, and gold bands, its nominal resistance value is 360 ohms with a tolerance of ± 5 percent. If a resistor is marked with red, orange, violet, black, and brown, its nominal resistance value is 237 ohms with a tolerance of ± 1 percent.

## Resistors in Series

**9** You can connect resistors in series. [Figure 1.3](#) shows two resistors in series.

**Figure 1.3**

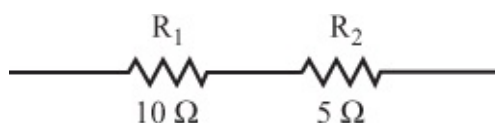

## Question

What is their total resistance? \_\_\_\_\_

## Answers


$$R_T = R_1 + R_2 = 10 \text{ ohms} + 5 \text{ ohms} = 15 \text{ ohms}$$

The total resistance is often called the *equivalent series resistance* and is denoted as  $R_{eq}$ .

# Resistors in Parallel

**10** You can connect resistors in parallel, as shown in [Figure 1.4](#).

[Figure 1.4](#)

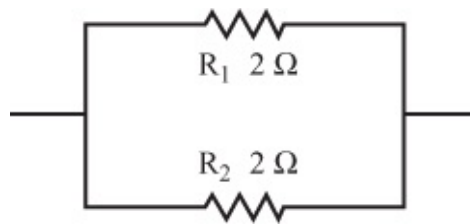

## Question

What is the total resistance here? \_\_\_\_\_

## Answers

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{2} + \frac{1}{2} = 1; \text{ thus } R_T = 1 \text{ ohm}$$

$R_T$  is often called the *equivalent parallel resistance*.

**11** The simple formula from problem 10 can be extended to include as many resistors as wanted.

## Question

What is the formula for three resistors in parallel? \_\_\_\_\_

## Answers

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

You often see this formula in the following form:

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

**12** In the following exercises, two resistors are connected in parallel.

## Questions

What is the total or equivalent resistance?

A.  $R_1 = 1 \text{ ohm}$ ,  $R_2 = 1 \text{ ohm}$

$R_T = \underline{\hspace{2cm}}$

B.  $R_1 = 1,000 \text{ ohms}$ ,  $R_2 = 500 \text{ ohms}$

$R_T = \underline{\hspace{2cm}}$

C.  $R_1 = 3,600 \text{ ohms}$ ,  $R_2 = 1,800 \text{ ohms}$

$R_T = \underline{\hspace{2cm}}$

## Answers

A. 0.5 ohms

B. 333 ohms

C. 1,200 ohms

$R_T$  is always smaller than the smallest of the resistors in parallel.

## Power

**13** When current flows through a resistor, it dissipates power, usually in the form of heat. Power expressed in terms of watts.

## Question

What is the formula for power?  $\underline{\hspace{2cm}}$

## Answers

There are three formulas for calculating power:

$$P = VI \text{ or } P = I^2R \text{ or } P = \frac{V^2}{R}$$

**14** The first formula shown in problem 13 allows power to be calculated when only the voltage and current are known.

## Questions

What is the power dissipated by a resistor for the following voltage and current values?

A.  $V = 10 \text{ volts}$ ,  $I = 3 \text{ amperes}$

$P = \underline{\hspace{2cm}}$

B.  $V = 100 \text{ volts}$ ,  $I = 5 \text{ amperes}$

$P = \underline{\hspace{2cm}}$

C.  $V = 120 \text{ volts}$ ,  $I = 10 \text{ amperes}$

$P = \underline{\hspace{2cm}}$

## Answers

- A. 30 watts.
- B. 500 watts, or 0.5 kW. (The abbreviation kW indicates kilowatts.)
- C. 1,200 watts, or 1.2 kW.

**15** The second formula shown in problem 13 allows power to be calculated when only the current and resistance are known.

## Questions

What is the power dissipated by a resistor given the following resistance and current values?

- A.  $R = 20 \text{ ohm}$ ,  $I = 0.5 \text{ ampere}$   
 $P = \underline{\hspace{2cm}}$
- B.  $R = 560 \text{ ohms}$ ,  $I = 0.02 \text{ ampere}$   
 $P = \underline{\hspace{2cm}}$
- C.  $V = 1 \text{ volt}$ ,  $R = 2 \text{ ohms}$   
 $P = \underline{\hspace{2cm}}$
- D.  $V = 2 \text{ volt}$ ,  $R = 10 \text{ ohms}$   
 $P = \underline{\hspace{2cm}}$

## Answers

- A. 5 watts
- B. 0.224 watts
- C. 0.5 watts
- D. 0.4 watts

**16** Resistors used in electronics generally are manufactured in standard values with regard to resistance and power rating. Appendix D shows a table of standard resistance values for 0.25- and 0.05-watt resistors. Quite often, when a certain resistance value is needed in a circuit, you must choose the closest standard value. This is the case in several examples in this book.

You must also choose a resistor with the power rating in mind. Never place a resistor in a circuit that requires that resistor to dissipate more power than its rating specifies.

## Questions

If standard power ratings for carbon film resistors are 1/8, 1/4, 1/2, 1, and 2 watts, what power ratings should be selected for the resistors that were used for the calculations in problem 15?

- A. For 5 watts \_\_\_\_\_
- B. For 0.224 watts \_\_\_\_\_
- C. For 0.5 watts \_\_\_\_\_
- D. For 0.4 watts \_\_\_\_\_



## Answers

- A. 5 watt (or greater)
- B. 1/4 watt (or greater)
- C. 1/2 watt (or greater)
- D. 1/2 watt (or greater)

Most electronics circuits use low-power carbon film resistors. For higher-power levels (such as the watt requirement in question A), other types of resistors are available.

## Small Currents

**17** Although currents much larger than 1 ampere are used in heavy industrial equipment, in most electronic circuits, only fractions of an ampere are required.

### Questions

- A. What is the meaning of the term *milliampere*? \_\_\_\_\_
- B. What does the term *microampere* mean? \_\_\_\_\_

### Answers

- A. A milliampere is one-thousandth of an ampere (that is, 1/1000 or 0.001 amperes). It is abbreviated mA.
- B. A microampere is one-millionth of an ampere (that is, 1/1,000,000 or 0.000001 amperes). It is abbreviated  $\mu\text{A}$ .

**18** In electronics, the values of resistance normally encountered are quite high. Often, thousands of ohms and occasionally even millions of ohms are used.

### Questions

- A. What does  $\text{k}\Omega$  mean when it refers to a resistor? \_\_\_\_\_
- B. What does  $\text{M}\Omega$  mean when it refers to a resistor? \_\_\_\_\_

### Answers

- A. Kilohm ( $\text{k} = \text{kilo}$ ,  $\Omega = \text{ohm}$ ). The resistance value is thousands of ohms. Thus,  $1\text{ k}\Omega = 1,000\text{ ohms}$ ,  $2\text{ k}\Omega = 2,000\text{ ohms}$ , and  $5.6\text{ k}\Omega = 5,600\text{ ohms}$ .
- B. Megohm ( $\text{M} = \text{mega}$ ,  $\Omega = \text{ohm}$ ). The resistance value is millions of ohms. Thus,  $1\text{ M}\Omega = 1,000,000\text{ ohms}$ , and  $2.2\text{ M}\Omega = 2,200,000\text{ ohms}$ .

**19** The following exercise is typical of many performed in transistor circuits. In this example, 10 volts is applied across a resistor, and 5 mA of current is required to flow through the resistor.

## Questions

What value of resistance must be used and what power will it dissipate?

R = \_\_\_\_\_ P = \_\_\_\_\_

## Answers

$$R = \frac{V}{I} = \frac{6 \text{ volts}}{5 \text{ mA}} = \frac{6}{0.005} = 1200 \text{ ohms} = 1.2 \text{ k}\Omega$$

$$P = V \times I = 6 \times 0.005 = 0.030 \text{ watts} = 30 \text{ mW}$$

**20** Now, try these two simple examples.

## Questions

What is the missing value?

**A.** 50 volts and 10 mA. Find the resistance. \_\_\_\_\_

**B.** 1 volt and 1 M $\Omega$ . Find the current. \_\_\_\_\_

## Answers

**A.** 5 k $\Omega$

**B.** 1  $\mu$ A

# The Graph of Resistance

**21** The voltage drop across a resistor and the current flowing through it can be plotted on a simple graph. This graph is called a *V-I curve*.

Consider a simple circuit in which a battery is connected across a 1 k $\Omega$  resistor.

## Questions

**A.** Find the current flowing if a 10-volt battery is used. \_\_\_\_\_

**B.** Find the current when a 1-volt battery is used. \_\_\_\_\_

**C.** Now find the current when a 20-volt battery is used. \_\_\_\_\_

## Answers


**A.** 10 mA

**B.** 1 mA

**C.** 20 mA

**22** Plot the points of battery voltage and current flow from problem 21 on the graph shown [Figure 1.5](#), and connect them together.

[Figure 1.5](#)

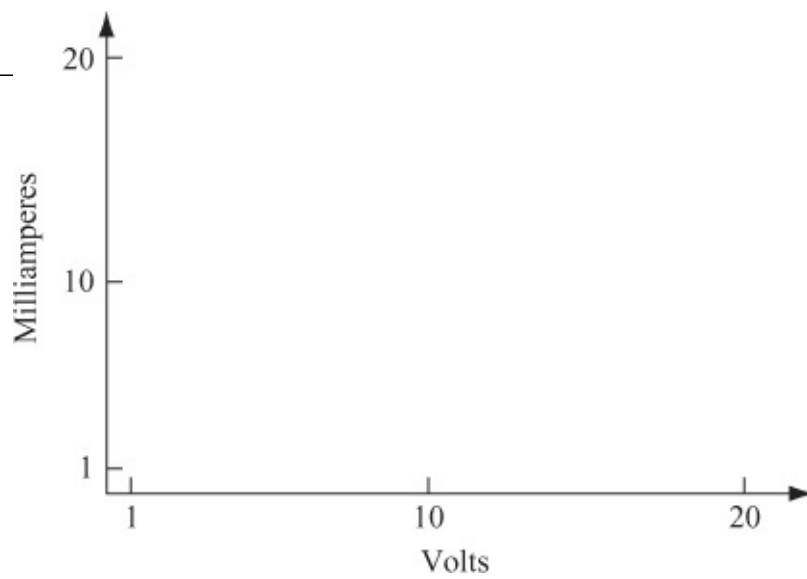


## Question

What would the slope of this line be equal to? \_\_\_\_\_

## Answers

You should have drawn a straight line, as in the graph shown in [Figure 1.6](#).

### Figure 1.6

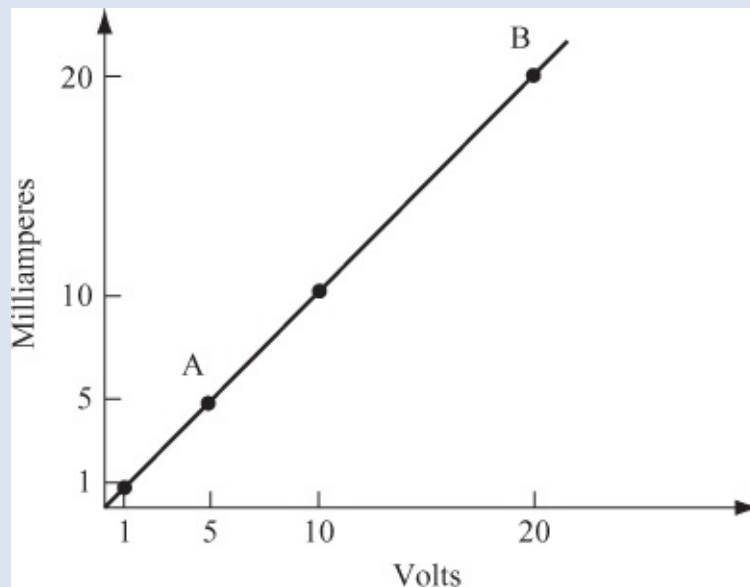

Sometimes you need to calculate the slope of the line on a graph. To do this, pick two points and call them A and B.

- For point A, let  $V = 5$  volts and  $I = 5$  mA
- For point B, let  $V = 20$  volts and  $I = 20$  mA

The slope can be calculated with the following formula:

$$\text{Slope} = \frac{V_B - V_A}{I_B - I_A} = \frac{20 \text{ volts} - 5 \text{ volts}}{20 \text{ mA} - 5 \text{ mA}} = \frac{15 \text{ volts}}{15 \text{ mA}} = \frac{15 \text{ volts}}{0.015 \text{ ampere}} = 1 \text{ k} \Omega$$


In other words, the slope of the line is equal to the resistance.

Later, you learn about V-I curves for other components. They have several uses, and often they are not straight lines.

# The Voltage Divider

**23** The circuit shown in [Figure 1.7](#) is called a *voltage divider*. It is the basis for many important theoretical and practical ideas you encounter throughout the entire field of electronics.

[Figure 1.7](#)

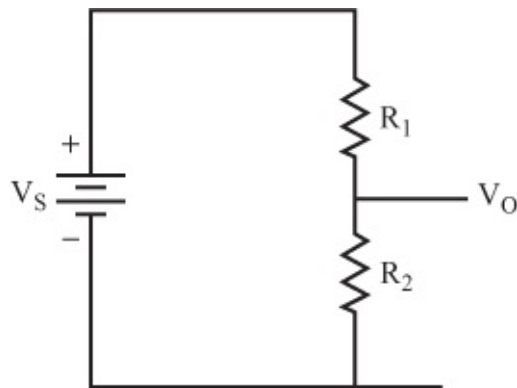

The object of this circuit is to create an output voltage ( $V_O$ ) that you can control based upon the two resistors and the input voltage.  $V_O$  is also the *voltage drop* across  $R_2$ .

## Question

What is the formula for  $V_O$ ? \_\_\_\_\_

## Answers

$$V_o = V_s \times \frac{R_2}{R_1 + R_2}$$


$R_1 + R_2 = R_T$ , the total resistance of the circuit.

**24** A simple example can demonstrate the use of this formula.

## Question

For the circuit shown in [Figure 1.8](#), what is  $V_O$ ? \_\_\_\_\_

[Figure 1.8](#)

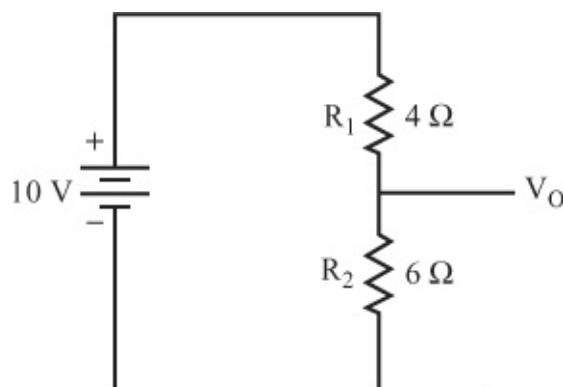

## Answers

$$\begin{aligned}V_O &= V_S \times \frac{R_2}{R_1 + R_2} \\ &= 10 \times \frac{6}{4 + 6} \\ &= 10 \times \frac{6}{10} \\ &= 6 \text{ volts}\end{aligned}$$

**25** Now, try these problems.

## Questions

What is the output voltage for each combination of supply voltage and resistance?

**A.**  $V_S = 1$  volt,  $R_1 = 1$  ohm,  $R_2 = 1$  ohm

$$V_0 = \underline{\hspace{2cm}}$$

**B.**  $V_S = 6$  volts,  $R_1 = 4$  ohms,  $R_2 = 2$  ohms

$$V_0 = \underline{\hspace{2cm}}$$

**C.**  $V_S = 10$  volts,  $R_1 = 3.3$  k $\Omega$ ,  $R_2 = 5.6$  k $\Omega$

$$V_0 = \underline{\hspace{2cm}}$$

**D.**  $V_S = 28$  volts,  $R_1 = 22$  k $\Omega$ ,  $R_2 = 6.2$  k $\Omega$

$$V_0 = \underline{\hspace{2cm}}$$

## Answers

**A.** 0.5 volts

**B.** 2 volts

**C.** 6.3 volts

**D.** 6.16 volts

**26** The output voltage from the voltage divider is always less than the applied voltage. Voltage dividers are often used to apply specific voltages to different components in a circuit. Use the voltage divider equation to answer the following questions.

## Questions

**A.** What is the voltage drop across the 22 k $\Omega$  resistor for question D of problem 25?

\_\_\_\_\_

**B.** What total voltage do you get if you add this voltage drop to the voltage drop across the 6.2 k $\Omega$  resistor? \_\_\_\_\_

## Answers

A. 21.84 volts


B. The sum is 28 volts.

The voltages across the two resistors add up to the supply voltage. This is an example of *Kirchhoff's Voltage Law (KVL)*, which simply means that the voltage supplied to a circuit must equal the sum of the voltage drops in the circuit. In this book, KVL is often used without actual reference to the law.

Also the voltage drop across a resistor is proportional to the resistor's value. Therefore, if one resistor has a greater value than another in a series circuit, the voltage drop across the higher-value resistor is greater.
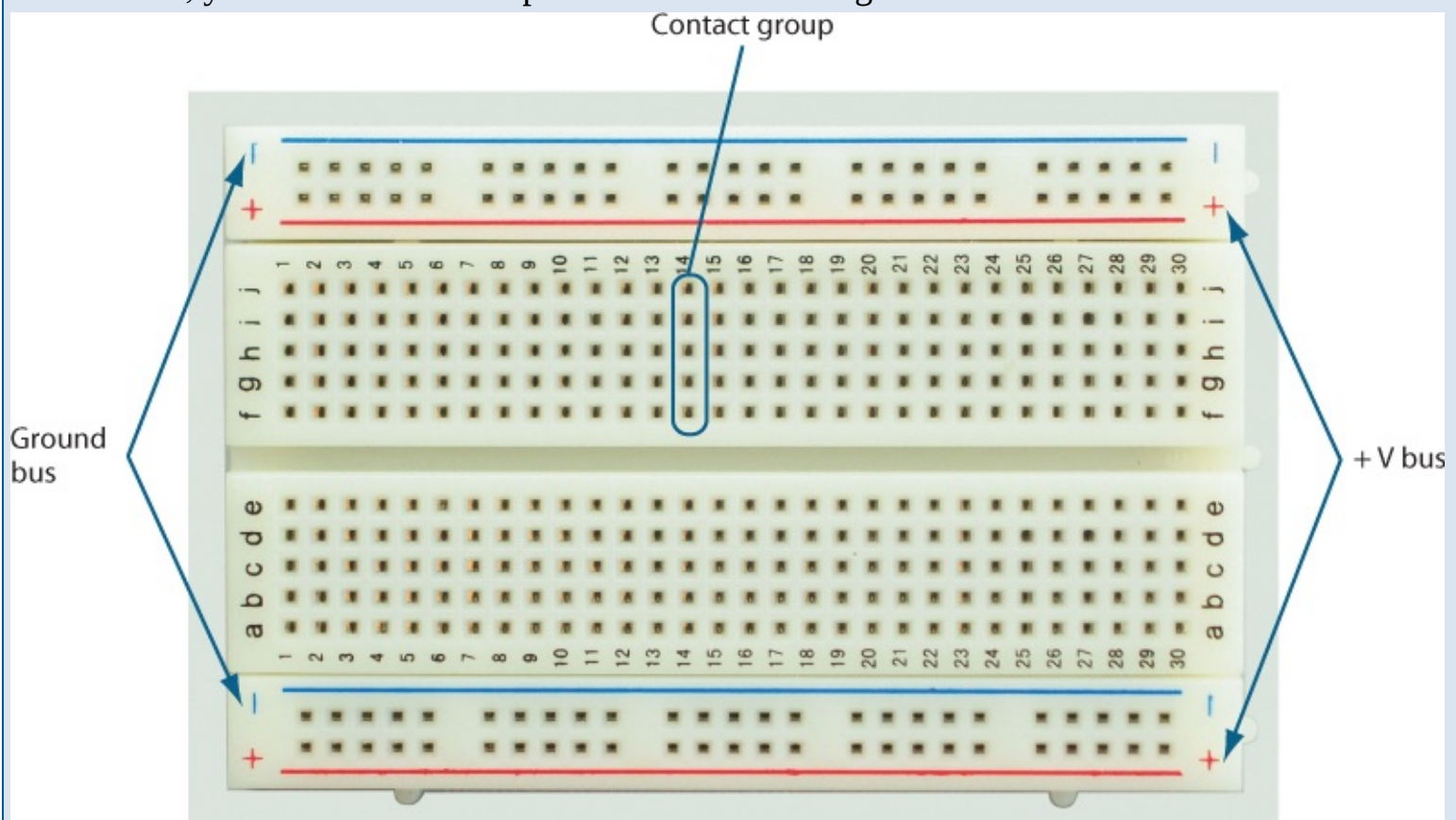
## Using Breadboards

A convenient way to create a prototype of an electronic circuit to verify that it works is to build it on a *breadboard*. You can use breadboards to build the circuits used in the projects later in this book. As shown in the following figure, a breadboard is a sheet of plastic with several contact holes. You use these holes to connect electronic components in a circuit. After you verify that a circuit works with this method, you can then create a permanent circuit using soldered connections.




Breadboards contain metal strips arranged in a pattern under the contact holes, which are used to connect groups of contacts together. Each group of five contact holes in a vertical line (such as the group circled in the figure) is connected by these metal strips. Any components plugged into one of these five contact holes are, therefore, electrically connected.

Each row of contact holes marked by a "+" or "-" are connected by these metal strips. The rows marked "+" are connected to the positive terminal of the battery or power supply and are referred to as the *+V bus*. The rows marked "-" are connected to the negative terminal of the battery or power supply.



supply and are referred to as the *ground bus*. The 1V buses and ground buses running along the top and bottom of the breadboard make it easy to connect any component in a circuit with a short piece of wire called a *jumper wire*. Jumper wires are typically made of 22-gauge solid wire with approximately 1/4 inch of insulation stripped off each end.

The following figure shows a voltage divider circuit assembled on a breadboard. One end of  $R_1$  is inserted into a group of contact holes that is also connected by a jumper wire to the 1V bus. The other end of  $R_1$  is inserted into the same group of contact holes that contains one end of  $R_2$ . The other end of  $R_2$  is inserted into a group of contact holes that is also connected by a jumper wire to the ground bus. In this example, a 1.5 k $\Omega$  resistor was used for  $R_1$ , and a 5.1 k $\Omega$  resistor was used for  $R_2$ .

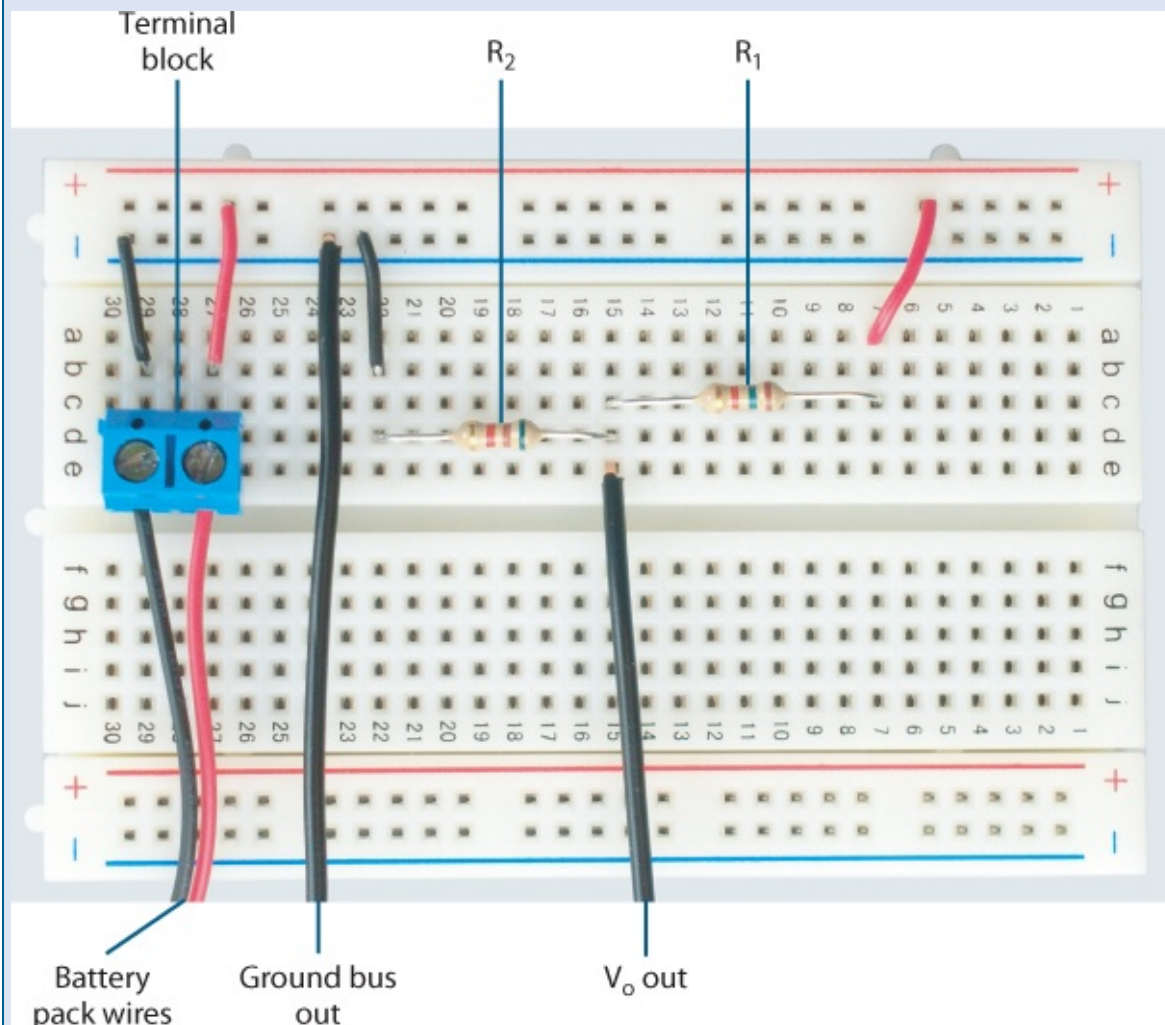


A *terminal block* is used to connect the battery pack to the breadboard because the wires supplied with battery packs (which are stranded wire) can't be inserted directly into breadboard contact holes. The red wire from a battery pack is attached to the side of the terminal block that is inserted into a group of contact holes, which is also connected by a jumper wire to the 1V bus. The black wire from the battery pack is attached to the side of the terminal block that is inserted into a group of contact holes which is also connected by a jumper wire to the ground bus.

To connect the output voltage,  $V_o$ , to a multimeter or a downstream circuit, two additional connections are needed. One end of a jumper wire is inserted in the same group of contact holes that contain both  $R_1$  and  $R_2$  to supply  $V_o$ . One end of another jumper wire is inserted in a contact hole in the ground bus to provide an electrical contact to the negative side of the battery. When connecting test equipment to the breadboard, you should use a 20-gauge jumper wire because sometimes the 22-gauge wire is pulled out of the board when attaching test probes.

# The Current Divider

**27** In the circuit shown in [Figure 1.9](#), the current splits or divides between the two resistors that are connected in parallel.

**Figure 1.9**

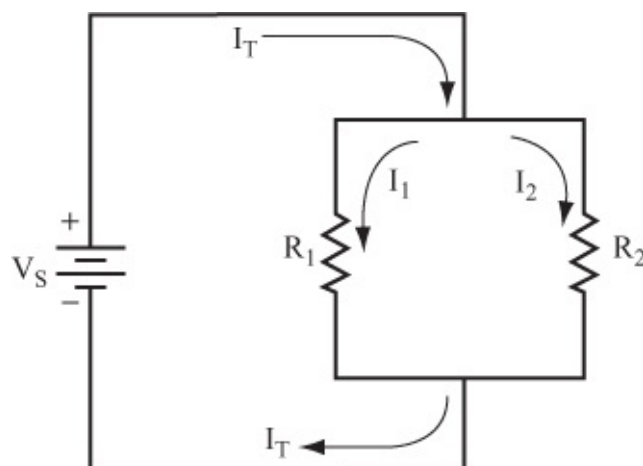

$I_T$  splits into the individual currents  $I_1$  and  $I_2$ , and then these recombine to form  $I_T$ .

## Questions

Which of the following relationships are valid for this circuit?

- A.  $V_S = R_1 I_1$
- B.  $V_S = R_2 I_2$
- C.  $R_1 I_1 = R_2 I_2$
- D.  $I_1 / I_2 = R_2 / R_1$

## Answers

All of them are valid.

**28** When solving current divider problems, follow these steps:

1. Set up the ratio of the resistors and currents:

$$I_1 / I_2 = R_2 / R_1$$

2. Rearrange the ratio to give  $I_2$  in terms of  $I_1$ :

$$I_2 = I_1 \times \frac{R_1}{R_2}$$

3. From the fact that  $I_T = I_1 + I_2$ , express  $I_T$  in terms of  $I_1$  only.
4. Now, find  $I_1$ .
5. Now, find the remaining current ( $I_2$ ).



- [read A Cast-Off Coven \(Witchcraft Mystery, Book 2\)](#)
- [download online Bordered Lives: Transgender Portraits from Mexico](#)
- [An Introduction to Japanese - Syntax, Grammar & Language book](#)
- [read online Shadow of Power \(Paul Madriani Series, Book 9\) here](#)
  
- <http://damianfoster.com/books/Anti-Badiou--The-Introduction-of-Maoism-into-Philosophy.pdf>
- <http://berttrotman.com/library/Bordered-Lives--Transgender-Portraits-from-Mexico.pdf>
- <http://paulczajak.com/?library/An-Introduction-to-Japanese---Syntax--Grammar---Language.pdf>
- <http://academialanguagebar.com/?ebooks/Shadow-of-Power--Paul-Madriani-Series--Book-9-.pdf>